

# Chapter 28 Fundamentals of Circuits

David Robinson

## Kirchhoff's Laws and the Basic Circuit

Because charge is conserved, for junctions,

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

Because energy is conserved, a charge that moves around a closed path has  $\Delta U_{\text{elec}} = 0$ .

$$\Delta V_{\text{loop}} = \sum (\Delta V)_i = 0$$

## Energy and Power

The rate at which the battery supplies energy to the charges is

$$P = \Delta V_R \times I = I^2 \times R = \frac{(\Delta V_R)^2}{R}$$

where  $P$  is the power in watts,  $V$  is the voltage,  $I$  is the current, and  $R$  is the resistance.

## Series Resistors

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \cdots \quad (\text{sequential resistors})$$

$$\Delta V_{\text{eq}} = \Delta V_1 + \Delta V_2 + \Delta V_3 + \cdots \quad (\text{sequential resistors})$$

## Real Batteries

Real batteries provide a slight resistance called an internal resistance.

When a connection of very low or zero resistance is made between two points in a circuit that are normally separated by a higher resistance, a short circuit is formed which shorts out the battery. If the battery were ideal, shorting it with zero resistance would cause the current to be  $I = \varepsilon/0 = \text{inf}$ . The current cannot really become infinite since the battery has an internal resistance  $r$ .

$$I_{\text{short}} = \frac{\varepsilon}{r}$$

## Parallel Resistors

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \cdots \quad (\text{parallel resistors})$$

## Grounded Circuits

A circuit connected to the earth is said to be grounded, and the wire is called the ground wire. There isn't a second wire so there is no current in the wire, it is just used as a common reference point for the potential but does not in any way change how the circuit functions.

## RC Circuits

Circuits with resistors and capacitors are called RC circuits.

If we use  $\tau = RC$  as the time constant for how much the capacitor has been discharged,

$$Q = Q_0 e^{-t/\tau}$$

$$\Delta V_C = \Delta V_0 e^{-t/\tau}$$

There's no specific time at which the capacitor has been completely discharged, because  $\Delta V$  approaches zero asymptotically, but the voltage and current will drop below 1% of their initial values at some point.

The same time constant can be used for charging a capacitor,

$$\Delta V = \varepsilon(1 - e^{-t/\tau})$$

$$I = I_0 e^{-t/\tau} \quad ((\text{capacitor charging}))$$